

Assignment 3.1 - Basics of Logic Design

09/10/2024

Late

30/30 Points

Attempt 1



Review Feedback

01/12/2024

Attempt 1 Score:

30/30

Add Comment

Anonymous Grading: **no**

Unlimited Attempts Allowed

07/10/2024

Details

Given the exercises below, **Build the Truth Table and Draw the circuit representation.**

$$1. X = A + BC$$

$$2. X = A(B + D)$$

$$3. X = W(V + Y)Z$$

$$4. X = PT(P + Z)$$

$$5. X = (A + B)(A + C)$$

$$6. X = (A + B)C$$

$$7. X = A + BC + D$$

$$8. X = AB + AC$$

$$9. X = (A + B)(C + D)C$$

Submission:

.pdf, .doc





(<https://slcc.instructure.com/courses/1004604/modules/items/25472224>)



Attempt 1 of 1
(<https://slcc.instructure.com/courses/1004604/modules/item>)