

# Lab 5. LED Bar Graph

04/11/2024

Missing **0/15 Points**

Attempt 1



Review Feedback

Offline Score:

**0/15**

Add Comment

Anonymous Grading: **no**


## Unlimited Attempts Allowed

### Details

The bar graph - a series of LEDs in a line, such as you see on an audio display - is a common hardware display for analog sensors. It's made up of a series of LEDs in a row, an analog input like a potentiometer, and a little code in between. You can buy multi-LED bar graph displays fairly cheaply, like [this one](http://www.digikey.com/product-detail/en/MV54164/1080-1183-ND/2675674). This tutorial demonstrates how to control a series of LEDs in a row, but can be applied to any series of digital outputs.

This tutorial borrows from the [For Loop and Arrays](https://www.arduino.cc/en/Tutorial/Loop) tutorial as well as the [Analog Input](https://www.arduino.cc/en/Tutorial/BuiltInExamples/AnalogInput) tutorial.

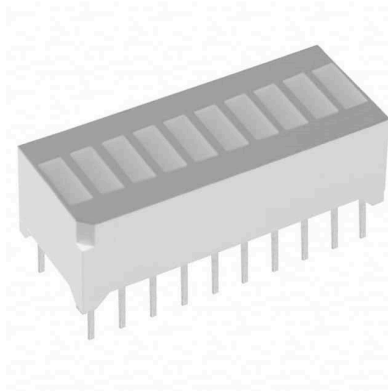
<http://www.arduino.cc/en/Tutorial/BarGraph>



## Hardware Required

- Arduino Board
- LED bar graph display or 10 LEDs
- Potentiometer
- 10 220 ohm resistors
- hook-up wires
- breadboard

## Circuit

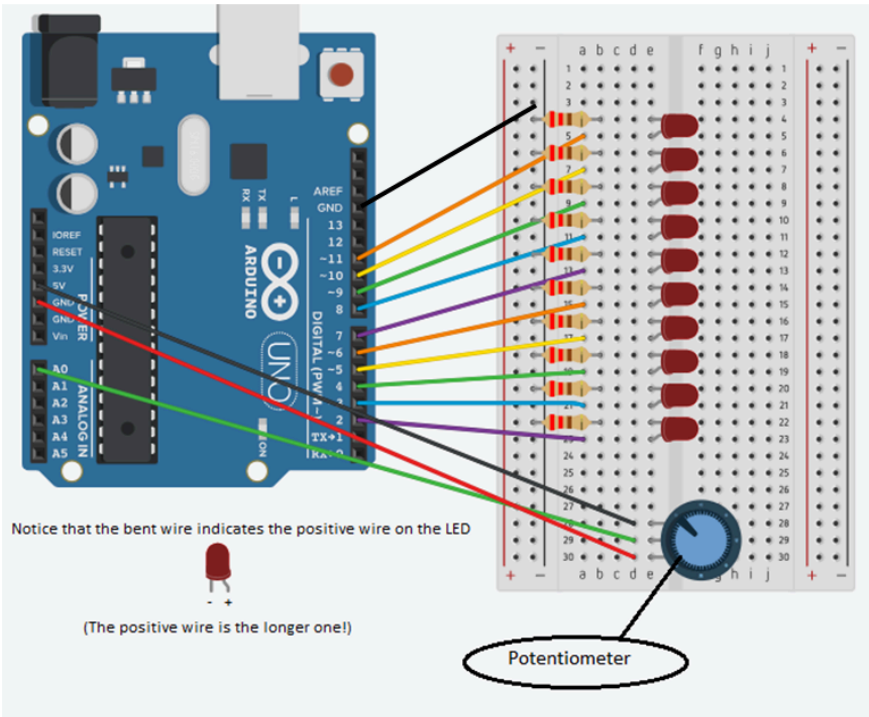

Code:

[barGraph.ino \(https://slcc.instructure.com/courses/1004604/files/165676767?wrap=1\)](https://slcc.instructure.com/courses/1004604/files/165676767?wrap=1). [↓](https://slcc.instructure.com/courses/1004604/files/165676767/download?download_frd=1)  
([https://slcc.instructure.com/courses/1004604/files/165676767/download?download\\_frd=1](https://slcc.instructure.com/courses/1004604/files/165676767/download?download_frd=1))

Submission:

Submit the video recording

View Rubric


Lab 5. Lab Bar Graph

Criteria	Ratings					Pts
Description of criterion <a href="#">view longer description</a>	5 pts Well done!	3 pts Close The implementation slightly differs from the instructions.	2 pts Getting There The implementation shows two slight differences or one larger difference from the implementation.	1 pts Needs Improvement The implementation differs in significant ways from the instructions.	0 pts Insufficient The circuit is missing or it shows little resemblance with the instructions.	/ 5 pts
Output <a href="#">view longer description</a>	10 pts Well done!		0 pts Differs from expected output			/ 10 pts
Total Points: 0						

Choose a submission type



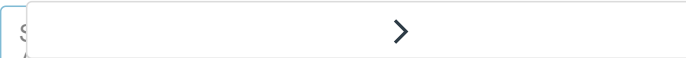(<https://slcc.instructure.com/courses/1004604/modules/items/25472216>)



Assignment  
(<https://slcc.instructure.com/courses/1004604/modules/items/25472217>)